

ELEC3608 - Computer Architecture

Assignment Report - Pipelined Processor

Kevin Nguyen - 311254039 and Khanh Nguyen - 311253865

Part 1: Implementation of a hazard-free function `nfib(unsigned int n)`

Design and Implementation

This part of the assignment required the `nfib` function to be written and tested on the pipelined PS_SPIM processor. The `nfib` function is limited to the available instructions in the given processor.

The `nfib(unsigned int n)` function returns the largest i for which $\text{fib}(i) \leq n$.
(e.g. `nfib(0)=0`, `nfib(1)=2`, `nfib(100,000)=25`)

Our initial design of `nfib(n)` was to calculate each fibonacci number upwards and count how many time we called `fib(n)`. We had previously implemented a recursive fibonacci function in MIPS, however it exponentially slowed down as the input value increased. There was also mentions that there is a lack of stack memory in the given processor. This lead us to a sequential design as seen in **Figure 1**, which was more simplistic and efficient.

```
function nfib(int n){
    int a = 0
    int b = 1
    int counter = 1
    int temp = 0

    while (b < n){
        temp = b
        b = a + b
        a = temp
        counter++
    }
    return counter
}
```

Figure 1: Pseudocode for `nfib(n)`

The pseudocode in **Figure 1** is our design of `nfib(n)`. We start by initialising variables `a` which is the placeholder for the previous fibonacci number, `b` which is the placeholder for the current fibonacci number, `counter` and `temp` which is a temporary variable used for swapping variables.

The function then loops until the current fibonacci number `b` is greater or equal to the input value `n`, each time calculating the next fibonacci number, rearranging the variables for the next loop and incrementing the counter. You can see that the fibonacci series is visible in the `b` row of the table in **Figure 2**.

a	0	1	1	2	3	5	8	13	21	34	55	89	144	233	...
b	1	1	2	3	5	8	13	21	34	55	89	144	233	377	...
temp	0	1	1	2	3	5	8	13	21	34	55	89	144	233	...
counter	1	2	3	4	5	6	7	8	9	10	11	12	13	14	...

Figure 2: Values of $nfib(n)$ at the start and after each loop

```
.data
msg1: .asciiz "Give a number: "
.text
.globl main
main:      li $s0, 0 #a = 0
          li $s1, 1  #b = 1
          li $s2, 0  #counter = 0
          li $a0, 123 #input
          addi $a0, $a0, 1

fib:  slt $t1, $s1, $a0
      beq $t1, $0, exit
      add $t0, $s1, $0    #t = b
      add $s1, $s0, $s1   #b = a+b
      add $s0, $t0, $0    #a = t
      addi $s2, $s2, 1
      j  fib

exit:      li $v0, 10
          syscall
```

Figure 3: MIPS assembly of $nfib(n)$ as written on Qtspim.exe

This was not compatible with the given PS_SPIM processor because:

- No i format instructions, initialised memory then load into registers
- To increment counter, because there is no i format, had to lw one of the registers with the value of 1 and used that to increment.
- To j instruction, used beq \$0, \$0, xx as unconditional jump
- Could not use slt so we used 'sub' and 'and' instead
 - Given value A and B, we did 'B - A' then AND it with 0x80000000. If B was smaller than A then B-A would return a negative result. This result AND 0x80000000 will return 0x80000000. However if it was a positive result, then it will return 0x0. So the result is always 0x0 when B is larger or equal to A and from there we can branch to the exit.

1	X"8C110004",	-- lw \$s1, 4(\$0)
2	X"8C040008",	-- lw \$a0, 8(\$0)
3	X"00008020",	-- add \$s0, \$zero, \$zero
4	X"00009020",	-- add \$s2, \$0, \$0
5	X"02242020",	-- add \$a0, \$a0, \$s1
6	X"8C130004",	-- lw \$s3, 4(\$0)
7	X"8C140010",	-- lw \$s4, 16(\$0)
8	X"02244822",	-- sub \$t1, \$s1, \$a0
9	X"00000000",	
10	X"00000000",	
11	X"01344824",	-- and \$t1, \$t1, \$s4
12	X"00000000",	
13	X"00000000",	
14	X"11200008",	-- beq \$t1, \$0, 24
15	X"00000000",	
16	X"00000000",	
17	X"02204020",	-- add \$t0, \$s1, \$0
18	X"02118820",	-- add \$s1, \$s0, \$s1
19	X"00000000",	
20	X"01008020",	-- add \$s0, \$t0, \$0
21	X"02729020",	-- add \$s2, \$s3, \$s2
22	X"1000FFF1",	-- beq \$0, \$0, -48 (PC + 4 - 60 = -56)
23	X"00000000",	
24	X"00000000",	
25	X"00000000",	

Figure 4: Translated MIPS assembly of *nfib(n)*

Lines 1 to 8 are arranged to avoid data hazards, e.g. Line 2 (lw \$a0, 8(\$0)) rd is equal to line 5 (add \$a0, \$a0, \$s1) rs (type 1a hazard) but line 2 is already in the write back stage when line 5 is in the instruction decode stage so no data hazard occurs. The same applies for line 1 and line 5 (lw \$s1, 4(\$0), add \$a0, \$a0, \$s1)

Lines 8, 11 and 14 is our conditional branch section and cannot be re arranged. So it data hazards are avoided by using 'nop'. It waits for the results to be written back before the instruction decode of the next operation occurs. Each beq instruction is followed by nops to prevent control hazards, as we cannot fetch the next instruction until we know the result of the beq operation.

 


Figure 5: Multi-Cycle pipeline diagram, lines 8 to 17

Changes to PS_SPIM (vhdl)

```

62 BEGIN
63 -- access instruction pointed to by current PC
64 -- and increment PC by 4. This is combinational
65
66 Instruction <= iram(CONV_INTEGER(PC(7 downto 2)));
67 PC_out <= (PC + 4);
68

```

Figure 6: Changes to ps_fetch.vhd included the PC being changed to accommodate for the larger nfib program (figure 4). This avoids any wrap around issues with the array when address is out of bounds. The size of the INST_MEM array was also changed to fit the instructions.

```

46
47 ALUop(1 downto 0) <= "01" WHEN Beq = '1' ELSE rformat & '0';
48

```

Figure 7: ps_control.vhd was changed so that the correct ALUop would be generated when we used beq.

The change in figure 7 was required so that the BEQ instruction would work.

```

26 architecture behavioral of memory is
27
28 TYPE DATA_RAM IS ARRAY (0 to 31) OF STD_LOGIC_VECTOR (31 DOWNTO 0);
29 SIGNAL dram: DATA_RAM := (
30     X"00000000",      --A value
31     X"00000001",      --B value
32     X"075bcd15",      -- 123456789 input
33     X"0000007B",      -- 123 input
34     X"80000000",      -- to get most sig. bit

```

Figure 8: ps_memory.vhd was initialised to the required values for the program. Only entries 0-4 were changed in the DATA_RAM array.

Testing

- **Testing Branch on Equal (BEQ) - generate correct aluOp and ALU_ctl**

Although this was not part of the assignment, the given BEQ instruction was not functional, so we had to fix and test it. To test the BEQ instruction we used the following program:

```
X"11200007", -- beq $t1, $0, 32
X"00000000", -- nop
X"00000000"  -- nop
```

Figure 9: Program to test BEQ

Expected Results:

1. the Branch_PC to be of value 0x20 (pc counter jumped up by 32)
2. the function opcode to be 0b000111
3. the ALUOp to be 0b01 if our changes in fig 7 are correct.

From there the correct ALU_ctl can be generated from function_opcode and ALUOp to tell ALU to subtract, expected value of ALU_ctl is 0b01.

Results:

 


Figure 10: Waveform of BEQ test program

As seen in figure 10 above, the BEQ test program passes and the instruction works as expected.

- **Testing nfib(n) - see if final register values are correct**

To test our nfib(n) function, we used the following test program, we ran it and had a look at the final values of the registers.

```

X"8C110004",      -- lw $s1, 4($0)
X"8C040008",      -- lw $a0, 8($0)
X"00008020",      -- add $s0, $zero, $zero
X"00009020",      -- add $s2, $0, $0
X"02242020",      -- add $a0, $a0, $s1
X"8C130004",      -- lw $s3, 4($0)
X"8C140010",      -- lw $s4, 16($0)
X"02244822",      -- sub $t1, $s1, $a0
X"00000000",
X"00000000",
X"01344824",      -- and $t1, $t1, $s4
X"00000000",
X"00000000",
X"11200008",      -- beq $t1, $0, 32 (PC + 4 + 28 = 32)
X"00000000",
X"00000000",
X"02204020",      -- add $t0, $s1, $0
X"02118820",      -- add $s1, $s0, $s1
X"00000000",
X"01008020",      -- add $s0, $t0, $0
X"02729020",      -- add $s2, $s3, $s2
X"1000FFF1",      -- beq $0, $0, -54 (PC + 4 - 60 = -54)
X"00000000",
X"00000000",
X"00000000"

```

Figure 11: Test program for nfib(n)

Expected Results:

- register \$s2 (=\$18) to contain the value 40

Results:

	Msgs				
register_array	{00000000} {11111111}...	{00000000} {11111111} {22222222} {33333333} {0}			
(0)	00000000	00000000			
(1)	11111111	11111111			
(2)	22222222	22222222			
(3)	33333333	33333333			
(4)	075BCD16	075BCD16			
(5)	55555555	55555555			
(6)	66666666	66666666			
(7)	77777777	77777777			
(8)	06197ECB	06197ECB			
(9)	00000000	00000000			
(10)	2222222A	2222222A			
(11)	3333333A	3333333A			
(12)	4444444A	4444444A			
(13)	5555555A	5555555A			
(14)	6666666A	6666666A			
(15)	7777777A	7777777A			
(16)	06197ECB	06197ECB			
(17)	09DE8D6D	09DE8D6D			
(18)	00000028	00000028			
(19)	00000001	00000001			
(20)	80000000	80000000			
(21)	5555555B	5555555B			
(22)	6666666B	6666666B			
(23)	7777777B	7777777B			
(24)	000000BA	000000BA			
(25)	111111BA	111111BA			
(26)	222222BA	222222BA			
(27)	333333BA	333333BA			
(28)	444444BA	444444BA			
(29)	555555BA	555555BA			
(30)	666666BA	666666BA			
(31)	777777BA	777777BA			

Figure 12: Waveform results of simulation of *nfib(n)* test program

As seen above in figure 12:

- register \$4 containing our input 0x75BCD16 (123456789)
- register \$16 and \$17 are our a and b variables, respectively. B is our fib sequence
- register \$18 is our counter and we can see that it contains 0x28 (40), which is what we expected.

Part 2: Add slt and slti instructions to PS_SPIM, and modify nfib to use slt/slti.

Design and Implementation

This part of the assignment required the *set on less than* (SLT) and the *set on less than immediate* (STLI) instructions to be added to the PS_SPIM processor.

```
89 WHEN "111" => if(Ainput < Binput) then
90     ALU_internal <= X"00000001";
91 else
92     ALU_internal <= X"00000000";
93 end if;
```

Figure 13: In *ps_fetch.vhd*, the switch case is modified so that the correct value of either 1 or 0, depending on the result, is the output for the ALU when the slt operation is performed.

```
27 rformat    <= '1' WHEN Opcode = "000000" ELSE '0';
28 Lw         <= '1' WHEN Opcode = "100011" ELSE '0';
29 Sw         <= '1' WHEN Opcode = "101011" ELSE '0';
30 Beq        <= '1' WHEN Opcode = "000100" ELSE '0';
31 iformat    <= '1' WHEN Opcode = "001010" ELSE '0';
32 --
33 -- implement each output signal as the column of the truth
34 -- table which defines the control
35 --
36
37 RegDst <= rformat;
38 ALUSrc <= (lw or sw or iformat) ;
39
40 MemToReg <= lw ;
41 RegWrite <= (rformat or lw or iformat);
42 MemRead <= lw ;
43 MemWrite <= sw;
44 Branch <= beq;
45
```

Figure 14: Changes made to *ps_control.vhd*

We added an iformat flag to warn us when it is an i format instruction, edited RegWrite flag to work for i format instructions. This enables i format instructions to right back to register.

```
46
47 ALUOp(1 downto 0) <= "01" WHEN Beq = '1' ELSE
48     "11" WHEN iformat = '1' ELSE
49     "10" WHEN rformat = '1' ELSE
50     "00";
```

Figure 15: *ps_control.vhd*, new ALUOp logic to allow i format instructions.

For the changes we made to ps_control as seen in figure 15 will set ALUop = 0b11 for i format instructions. This is used for the SLTI instruction.

```

61     ALU_ctl( 0 ) <= '1' WHEN ALUOp = "11" ELSE ( Function_opcode( 0 ) OR Function_opcode( 3 ) ) AND ALUOp(1) ;
62     ALU_ctl( 1 ) <= '1' WHEN ALUOp = "11" ELSE ( NOT Function_opcode( 2 ) ) OR (NOT ALUOp( 1 ) );
63     ALU_ctl( 2 ) <= '1' WHEN ALUOp = "11" ELSE ( Function_opcode( 1 ) AND ALUOp( 1 ) ) OR ALUOp( 0 );
64

```

Figure 16: ps_control.vhd, new ALU_ctl logic to generate correct ALU_ctl signal when using slti

We then removed the AND logic in place for the SLT instruction in the nfib(n) function.

```

X"8C110004",    -- lw $s1, 4($0)
X"8C040008",    -- lw $a0, 8($0)
X"00008020",    -- add $s0, $zero, $zero
X"00009020",    -- add $s2, $0, $0
X"02242020",    -- add $a0, $a0, $s1
X"8C130004",    -- lw $s3, 4($0)
X"00000000",    -- nop
X"0224482A",    -- slt $t1, $s1, $a0
X"00000000",    -- nop
X"00000000",    -- nop
X"11200008",    -- beq $t1, $0, 32
X"00000000",    -- nop
X"00000000",    -- nop
X"02204020",    -- add $t0, $s1, $0
X"02118820",    -- add $s1, $s0, $s1
X"00000000",    -- nop
X"01008020",    -- add $s0, $t0, $0
X"02729020",    -- add $s2, $s3, $s2
X"1000FF4",     -- beq $0, $0, -48 (PC + 4 - 48 = -44)
X"00000000",    -- nop
X"00000000",    -- nop
X"00000000",    -- nop

```

Figure 17: Translated MIPS assembly of nfib(n) using slt

Testing

- **Testing slt**

To test set on less than (slt), we used the following test program:

```
X"0001102A",      -- slt $2, $0, $1
X"00000000",
X"00000000",
X"00000000",
X"00000000",
X"00000000"
```

Figure 18: Test program for set on less than

The registers are already initialised, register \$1 contains 0x11111111 and \$0 contains 0x0 so \$1 is larger.

Expected Results:

- regWrite = 1
- alu_result = 1
- ALUOp = 10
- ALUctl = 111
- reg \$2 to b 0x1

Result:

 


Figure 19: Waveform results from simulation of slt test program

As expected, we can see alu_result = 0b1 , ALU_ctl = 0b111, ALUOp = 10. Then we can see wb_RegWrite going high followed by the alu_result going into \$2.

- **Testing slti**

To test set on less than immediate (slti), we used the following test program:

```
X"2802007B",      -- slti $2, $0, 123
X"00000000",
X"00000000",
X"00000000",
X"00000000",
X"00000000"
```

Figure 20: Test program for set on less than immediate

since \$0 is 0, we expect results to be

regWrite = 1, alu_result = 1, ALUOp = 11 (since it is iformat) , ALUCtl = 111, reg \$2 to b 0x1.

Results:

 


Figure 21: Waveform result from simulation of test program

as expected, ALUOp = 11, ALU_ctl = 111, ALU_result = 0x1. Then we can see wb_RegWrite go high and then the value 0x1 being written into reg \$2

Testing the nfib(n) program with slt:

The test program for this part that was used for testing can be seen in figure 11.

Expected Results:

- the final register value of \$18 to be 0x28 (40).

Results:

 


Figure 22: Waveform result from simulation of test program nfib(n) with slt

Our results show reg \$18 containing 28, so it is working as planned. The results are the same as part one. Only difference being that it is faster.

Part 3: Forwarding

Design and Implementation

For this part of the assignment, we were required to implement forwarding for all R-type instructions implemented in the PS_SPIM processor along with the SLT/SLTI instructions so that they can proceed as early as possible.

We created a forward unit that is able to detect when a forward is necessary, where to forward to and what data to forward.

```
19 architecture behavioral of forward is
20     signal mem_fwd_rs, mem_fwd_rt, ex_fwd_rs, ex_fwd_rt: std_logic;
21 begin
22     ex_fwd_rs <= '0' when (ex_mem_rd = "00000") else
23                 ex_mem_regWrite when (ex_mem_rd = id_ex_rs) else
24                 '0';
25
26     ex_fwd_rt <= '0' when (ex_mem_rd = "00000") else
27                 ex_mem_regWrite when (ex_mem_rd = id_ex_rt) else
28                 '0';
29
30     mem_fwd_rs <= '0' when (mem_wb_rd = "00000") else
31                 '0' when (ex_fwd_rs = '1') else
32                 mem_wb_regWrite when (mem_wb_rd = id_ex_rs) else
33                 '0';
34
35     mem_fwd_rt <= '0' when (mem_wb_rd = "00000") else
36                 '0' when (ex_fwd_rt = '1') else
37                 mem_wb_regWrite when (mem_wb_rd = id_ex_rt) else
38                 '0';
39
40     forwardRs <= ex_fwd_rs & mem_fwd_rs;
41     forwardRt <= ex_fwd_rt & mem_fwd_rt;
42
43
44 end behavioral;
```

Figure 23: Behavior of the forward entity

Figure 23 shows the behavior of our forward unit. It uses the 4 hazard conditions:

- 1a. EX/MEM.RegisterRd = ID/EX.RegisterRs
- 1b. EX/MEM.RegisterRd = ID/EX.RegisterRt
- 2a. MEM/WB.RegisterRd = ID/EX.RegisterRs
- 2b. MEM/WB.RegisterRd = ID/EX.RegisterRt

To set the flags for either a forward from EX/MEM pipeline reg or a forward from MEM/WB pipeline reg.

In order to compare the Rs register in the ID/EX stage with the Rd register, we had to create some modifications so the Rs address would propagate through.

```

25  -- outputs
26  --
27  register_rs, register_rt :out std_logic_vector(31 downto 0);
28  Sign_extend :out std_logic_vector(31 downto 0);
29  wreg_rd, wreg_rt, wreg_rs : out std_logic_vector (4 downto 0));
30  end decode;
31

```

```

103  -- move possible write destinations to execute stage
104  wreg_rd <= instruction(15 downto 11);
105  wreg_rt <= instruction(20 downto 16);
106  wreg_rs <= instruction(25 downto 21);
107

```

Figure 24: Changes made in ps_decode.vhd, added output wreg_rs

```

4  entity pipe_reg2 is
5  port (id_MemToReg, id_RegWrite, id_MemWrite, id_MemRead: in std_logic;
6        id_ALUSrc, id_RegDst, clk, reset, id_branch : in std_logic;
7        id_ALUOp : in std_logic_vector(1 downto 0);
8        id_PC4: in std_logic_vector(31 downto 0);
9        id_register_rs, id_register_rt, id_sign_extend: in std_logic_vector(31 downto 0);
10       id_wreg_rd, id_wreg_rt, id_wreg_rs : in std_logic_vector(4 downto 0);
11
12       ex_MemToReg, ex_RegWrite, ex_MemWrite, ex_MemRead, ex_branch: out std_logic;
13       ex_ALUSrc, ex_RegDst : out std_logic;
14       ex_ALUOp : out std_logic_vector(1 downto 0);
15       ex_PC4: out std_logic_vector(31 downto 0);
16       ex_register_rs, ex_register_rt, ex_sign_extend: out std_logic_vector(31 downto 0);
17       ex_wreg_rd, ex_wreg_rt, ex_wreg_rs : out std_logic_vector(4 downto 0));
18  end pipe_reg2;
19
20

```

Figure 25: In pipe_reg2.vhd, we added in id_wreg_rs and ex_wreg_rs, lines 10 and 17 respectively. in_wreg_rs <= ex_wreg_rs

Now ps_execute.vhd needs to be changed to make forwarding work. It needs to know when to use the register values or the forwarded data for its inputs for the ALU. On top of that, it needs to know where the forwarded data is coming from, i.e. EX/MEM stage or MEM/WB stage.

```

-- compute the two ALU inputs
Ainput <=  fwd_data_wb when forwardRs(0) = '1' ELSE
           fwd_data_mem when forwardRs(1) = '1' ELSE
           register_rs;

-- ALU input mux
Binput <=  fwd_data_wb when forwardRt(0) = '1' ELSE
           fwd_data_mem when forwardRt(1) = '1' ELSE
           register_rt WHEN ( ALUSrc = '0' ) else
           Sign_extend(31 downto 0) when ALUSrc = '1' else
           X"BBBBBBBB";

```

Figure 26: the mux for the inputs of the ALU. Given the forward flags set by the unit, it will choose its inputs accordingly.

```

11 entity execute is
12 port(
13   --
14   -- inputs
15   --
16   PC4 : in std_logic_vector(31 downto 0);
17   forwardRs, forwardRt: in std_logic_vector (1 downto 0);
18   register_rs, register_rt, fwd_data_wb, fwd_data_mem :in std_logic_vector (31 downto 0);
19   Sign_extend :in std_logic_vector(31 downto 0);
20   ALUOp: in std_logic_vector(1 downto 0);
21   ALUSrc, RegDst : in std_logic;
22   wreg_rd, wreg_rt : in std_logic_vector(4 downto 0);
23
24   -- outputs

```

Figure 27: the added inputs , fwd_data_wb and fwd_data_mem, for ps_execute.vhd (line 18).

With all the entities modified and ready, we now must connect the forwarding unit in the top level entity.

Inside the top level entity, spim_pipe we added the forward unit in. Then did the necessary internal signals and port mapping.

```

36   -- forwarding unit
37   component forward
38   port(ex_mem_regWrite:      in std_logic;
39        mem_wb_regWrite:     in std_logic;
40        mem_wb_rd:           in std_logic_vector(4 downto 0);
41        ex_mem_rd:           in std_logic_vector(4 downto 0);
42        id_ex_rs:            in std_logic_vector(4 downto 0);
43        id_ex_rt:            in std_logic_vector(4 downto 0);
44        forwardRs:           out std_logic_vector(1 downto 0);
45        forwardRt:           out std_logic_vector(1 downto 0));
46   end component;

```

Figure 28: Forwarding component

```

230 --
231 -- FW
232 --
233 signal forwardRt, forwardRs : std_logic_vector(1 downto 0);
273 -- instantiate forwarding
274 forward_unit : forward
275 port map(
276     ex_mem_regWrite => mem_RegWrite,
277     mem_wb_regWrite => wb_RegWrite,
278     mem_wb_rd => wb_wreg_addr,
279     ex_mem_rd => mem_wreg_addr,
280     id_ex_rs => ex_wreg_rs,
281     id_ex_rt => ex_wreg_rt,
282     forwardRs => forwardRs,
283     forwardRt => forwardRt);

```

Figure 29: Portmap for the forwarding component

```

372 EX: execute -- instantiate the component EX?
373
374 port map(PC4 => ex_PC4,
375     forwardRs => forwardRs,
376     forwardRt => forwardRt,
377     fwd_data_wb => wb_alu_result,
378     fwd_data_mem => mem_alu_result,
379     register_rs => ex_register_rs,
380     register_rt => ex_register_rt,
381     sign_extend => ex_sign_extend,
382     RegDst => ex_RegDst,
383     ALUOp => ex_ALUOp,
384     ALUSrc => ex_ALUSrc,
385     alu_result => ex_alu_result,
386     wreg_rd => ex_wreg_rd,
387     wreg_rt => ex_wreg_rt,
388     wreg_address => ex_wreg_addr,
389     branch_pc => ex_branch_PC,
390     zero => ex_zero);
391

```

Figure 30: forwarding flags from the forward unit connected to EX component (line 375, 376).

The fwd_data_wb and fwd_data_mem registers take the alu_results from the MEM/WB stage and EX/MEM stage respectively.


```

322 port map(instruction => id_instruction,
323           memory_data => wb_memory_data,
324           alu_result => wb_alu_result,
325           RegWrite => wb_RegWrite,
326           MemToReg => wb_MemToReg,
327           reset => reset,
328           register_rs => id_register_rs,
329           register_rt => id_register_rt,
330           Sign_extend => id_Sign_extend,
331           wreg_address => wb_wreg_addr,
332           wreg_rd => id_wreg_rd,
333           wreg_rt => id_wreg_rt,
334           wreg_rs => id_wreg_rs
335         );

```

Figure 31: port map for decode component. *wreg_rs* passes the address to the internal signal *id_wreg_rs*.

```

337 id_ex: pipe_reg2 -- instantiate the pipeline register ID/EX
338 port map(clk => clock,
339 reset => reset,
340     id_branch => id_branch,
341     id_MemToReg => id_MemToReg,
342     id_RegWrite => id_RegWrite,
343     id_MemWrite => id_MemWrite,
344     id_MemRead => id_MemRead,
345     id_ALUSrc => id_ALUSrc,
346     id_RegDst => id_RegDst,
347     id_ALUOp => id_ALUOp,
348     id_PC4 => id_PC4,
349     id_register_rs => id_register_rs,
350     id_register_rt => id_register_rt,
351     id_sign_extend => id_sign_extend,
352     id_wreg_rd => id_wreg_rd,
353     id_wreg_rt => id_wreg_rt,
354     id_wreg_rs => id_wreg_rs,
355
356     ex_branch => ex_branch,
357     ex_MemToReg => ex_MemToReg,
358     ex_RegWrite => ex_RegWrite,
359     ex_MemWrite => ex_MemWrite,
360     ex_MemRead => ex_MemRead,
361     ex_ALUSrc => ex_ALUSrc,
362     ex_RegDst => ex_RegDst,
363     ex_ALUOp => ex_ALUOp,
364     ex_PC4 => ex_PC4,
365     ex_register_rs => ex_register_rs,
366     ex_register_rt => ex_register_rt,
367     ex_sign_extend => ex_sign_extend,
368     ex_wreg_rd => ex_wreg_rd,
369     ex_wreg_rt => ex_wreg_rt,
370     ex_wreg_rs => ex_wreg_rs);
371
372 EX: execute -- instantiate the component EX?

```

Figure 32: port map for ID/EX pipeline registers. Added in lines 354 and 370.

Testing

To test whether our forwarding unit works or not, we took the code from part 2 (figure 11) and removed all the nops. If the forwarding unit is performing as intended, then the results should be the same as part 2 but achieved in fewer clock cycles. We cannot remove all the nops however because we only forwarded R type instructions, so nops are still needed after beq instructions.

We used the following test program to test:

```
X"8C110004", -- lw $s1, 4($0)
X"8C040008", -- lw $a0, 8($0)
X"00008020", -- add $s0, $zero, $zero
X"00009020", -- add $s2, $0, $0
X"02242020", -- add $a0, $a0, $s1
X"8C130004", -- lw $s3, 4($0)
X"0224482A", -- slt $t1, $s1, $a0
X"11200007", -- beq $t1, $0, 28
X"00000000", -- nop
X"00000000", -- nop
X"02204020", -- add $t0, $s1, $0
X"02118820", -- add $s1, $s0, $s1
X"01008020", -- add $s0, $t0, $0
X"02729020", -- add $s2, $s3, $s2
X"1000FFF7", -- beq $0, $0, -28 (PC + 4 - 32 = -28)
X"00000000", -- nop
X"00000000", -- nop
X"00000000", -- nop
```

Figure 33: Test program for $nfib(n)$ with forwarding

We expect the results to be exactly the same as part 2. But we also expect to see the amount of clock cycles needed to achieve the result to be less than parts 1 and 2. That is register \$18 to contain 0x28 and cycles to compute > 617.

 


Figure 34: Result waveform of simulation of the test program with forwarding

As we can see, register \$18 contains the value 0x28. The amount of cycles to compute with the forwarding of all R type instructions is 494 cycles. This confirms that our forwarding unit is working as intended.

	Cycles to compute nfib(123)	Cycles to compute nfib(123456789)
Question 1	218	740
Question 2	182	617
Question 3	146	494

Figure 35: Cycles needed to compute $\text{nfib}(n)$, where $n = 123$ and 123456789

There is a significant speedup from Question 1 to Question 3 as seen in Figure 35.

We save 72 cycles for $\text{nfib}(123)$ with a **speedup of 1.4931**

We save 246 cycles for $\text{nfib}(123456789)$ with a **speedup of 1.4980**